

Bernd Geck, DB3GF / 9A8ABG Renate Flesch, DH3MBF DARC, Ortsverband Ulm P14 & Freising C04

Level of Presentation: Beginner

Topic: Emergency HAM System for Radio Amateurs

author: Bernd Geck



Career

- a decade at the army, followed by the University of Ulm
- at TI / PDS since 2006 to 2023, after 15 years in TWT TX design at Telefunken and BTS design at Siemens

Expertise

- power electronics and RF electronics

Fun facts:

- radio amateur DB3GF & DL0TI, homebrewing RF LDMOS amplifiers
- freediving instructor, just a single breath...



Part A – RF System, Components

12V / 13.8V Components



Considerations:

- reuse of existing RF components
- all RF components powered out of 12Vdc
- "portable", weight <20kg:(build with or without RF amplifier ?)
- tuner for undefined multiband antenna ("end fed" long wire is easy to use)
- isolated interface to PC adds digital modes (VARA)

findings at the attic: TRX: IC-706MKIIG, PSU: SPS 9600 (60A)

PA: RM HLA 300 plus, I/F: microHAM USB 3,

Tuner MFJ-994B (600W PEP) tiny ACER Aspire NetBook 9"



Part A – RF System, Open Frame Case

Console 49cm x 45cm x 27cm



first orientating placement



Considerations:

- leave some space for convection
- place components for proper RF path
- use sturdy wood 12mm ("multiplex"), here: used beech, heavy but solid
- place handles barycentric
- case is varnished for outdoor use (field day)
- rubber pads prevent from slipping



Part A – RF System, Mounting Components

Example TRX



a sketch always helps...



Considerations:

- use drive-in nuts (!)
- bolted connections are best connections (shock & vibration during transportation)
- think about service and dismantling, too



Part A – RF System, Grounding Components

Common Ground



central ground at RF out



Considerations:

- ground all components of RF path
- use central ground at RF output, here at auto tuner MFJ-994B
- short connection to earth via 10mm^2
- ground any generator as well (!)



Part A – RF System, Final Layout

Ready to Run:



Bill of Materials:

- 5" coaxial loudspeaker
- 12V/24V LED Osram ONYX, part B
- combo key, part C
- microHAM USB 3 interface
- auto tuner MFJ-994B
- IC-706MKIIG
- solid state PA RM HLA 300 plus
- power supply SPS 9600, 13V8 / 60A





7

Part B – 500mW LED

Brightness 500mW LED, Load Current <50mA:



LED in service position,

lighting the back,

or illuminating at night





Part C – Tiny Combo Key using Palm Radio

Another Finding at the Attic:



some basic steel ST37 (100mm x 100mm x 5mm = 400g), the shower gets a paint shop, and stove enameling 75c at the baking oven makes every housewife very happy...





Part C – Tiny Combo Key using Palm Radio

Talk with Your Fingers:



keyer and paddle,

DARC OV P14



protected and parked...



RF System On Air

Mains Operations 230Vac:



70W CW in Digi Mode, 300W PEP in SSB



and the back...





Part D – an Universal Power Concept 800W+

Electrical Specifications for Maximum Output Power:

- 300W RF peak power results in 50Apk (!);
 expect 30% to 40% continuous power in SSB using a compressor, so 20A cont for 50% TX/RX in contest expect 11A average current (13.8V x 11A = 152W !!!)
- 70W RF power in digi mode results in 23A cont; for 50% TX/RX expect 12A average current, NetBook adds another 2A worst case; average power consumption in digi mode up to 13.8V x 14A = 193W !!!
- battery operations for ten hours at maximum output needs an energy of 2kWh
- if conditions are fine switch off PA to stretch life time of battery = QRP if conditions are even better use IC-706 at 5W output power – or less...



Part D – an Universal Power Concept 800W+

Various Power Sources:

- mains operations is covered by switched mode power supply SPS 9600: this power supply uses power factor correction PFC and the pre boost allows wideband input range 170Vac to 264Vac supporting an electrical generator
- "portable" generator MXR3500 (3.1kWpk/2.8kWcont) is in house: weight 22kg, needs less than one liter ROZ91/95 per hour in economy mode; upper PFC allows economy mode (transient response vs. load transient RX/TX)
- any battery power, i.e. "portable" around 20kg = LiFePO4 24V / 100Ah; allows 10hrs+ operation, needs DC/DC converter for constant output voltage 13.8V,

such a step down solution could be solar buffered as well



Part D - DC/DC Converter 800W+, PMP31210 RevB

Built on PCB 31202 Rev A3



four layers, single side assembly, 152.6mm x 130.8mm x 16mm

DARC OV P14

Specifications:

- synchronous four phase buck converter
- interleaved operation provides lowest ripple
- full thermal solution, shielded metal case
- input voltage range 18Vdc to 58Vdc
- 50A+ continuous load current
- 70A peak current
- efficiency up to 98%
- output ripple <10mVpp
- transient response <3% for 90% transient
- gate drive control to attenuate RF noise
- link: <u>https://www.ti.com/tool/PMP31210</u>



PMP31210 Design Review – Solution by LM5143



Schematics PMP31210 Rev B, two controllers / four power stages

- single power stage (x4)
- DARC OV P14

- stacked 2x LM5143 to 4-phase design, IC allows adjustment of rise and fall times !
- full ripple rejection at 24V / 48V input, here duty cycle is around 25% / 50%
- high dynamic performance, transient response 400mVpk, so <3% for 90% load step 5A / 50A (RX/TX)
- 800W continuous output power, 1kW peak



PMP31210 Design Review – Interleaved Operation



four phase interleaved operation, 200W per phase

DARC OV P14

👋 Texas Instruments

PMP31210 Design Review – Dynamics

Dynamic performance PMP31210 Rev B Bode Plot, V_{IN} = V_{IN(nom)} 45 60 -90 (.) Loop Gain (dB) FPLEATOM Phase 86' 20 doo n -135 Crossover Frequency = 10.1 kHz FZESR -20 Phase Margin = 86 -40 -180 10 100 1000 10000 100000 1000000 2 ms/Div

load transient 90%, 5A to 50A transient response <400mV, less than 3% (!) Loop in frequency domain, PM > 80degs / GM < -15dB

Frequency (Hz)

DARC OV P14

💠 Texas Instruments

17

PMP31210 Design Review – Efficiency & Losses



PMP31210 Design Review – Heat Sink

Thermal Interface PCB 31202 Rev A3, at the end the mechanics solution





👋 Texas Instruments

PMP31210 Design Review – Thermal Results

PMP31210 Rev B, prototype under test at ambient temperature +23c

Output Current	Hottest Spot HS FET Q6 NVMFS5C456, pure PCB	Hottest Spot with Airflow 0.5m/s1m/s, pure PCB	Hottest Spot, just mounted Aluminum <mark>Adapter</mark> , 150mm x 75mm x 5mm	added <mark>Heatsink</mark> to adapter, FISCHER, SK 58 75 SA
10 A	35.3°C	n/a	n/a	n/a
20 A	42.8°C	n/a	n/a	n/a
30 A	52.4°C	n/a	49.8°C	47.7°C
40 A	65.4°C	n/a	60.4°C	56.1°C
50 A	81.4°C	45.4°C	73.5°C	66.4°C
60 A	n/a	52.5°C	89.6°C	77.6°C

Remember: even a small air flow helps more than a big heat sink !





PMP31210 Design Review – Thermal Results

PMP31210 Rev B inside shielded metal case at 23c ambient



test set up – equipment at it's limits...



ten hours continuous operation...





Part D – Low Noise NetBook Supply

DC/DC Adapter Input 13.8V to Output 17V/19V:

- an old NetBook ACER Aspire is reused to support various digital modes; beneficial is the low power consumption < 30W of such a 9" portable PC
- despite it's 3s battery (12.6Vmax / 11.1Vtyp) the DC voltage of 13.8V is NOT sufficient to drive the PC ! The internal watchdog sets the threshold to 16V+, the AC adapter itself provides 19V
- next task is a cost effective but efficient DC/DC boost converter to provide 17Vdc to the PC; worst case current consumption while charging battery and executing a test software has been measured around 1.4A; targeting an efficiency 95% for a non synchronous topology this PC adds up to 1.95A to the 13.8V bus



Part D - DC/DC Converter 30W+, PMP31242 RevA

Built on PCB 30722



four layers, double side assembly,

DARC OV P14 × 15mm

Specifications:

- non synchronous step up (= boost) converter
- high and flat efficiency
- shielded metal case, low EMI needed
- input voltage range 8.5Vdc to 17Vdc
- 1.5A continuous load current
- 2.5A peak current
- efficiency up to 96% at load current 1A to
- 2.5A
- output ripple <10mVpp
- reflected input ripple <10mVpp
- standby current <1mA, here 600uA
- link: https://www.ti.com/tool/PMP31242

PMP31242 Design Review – Solution by LM5155

Schematics PMP31242 Rev A



30W+ boost converter

- used LM5155/56
- added RF input filter
- added RF output filter
- RC damping at rectifier
- Fsw 385kHz, harmonics out of band i.e. f(8) 3465kHz f(9) 3850kHz





PMP31242 Design Review – Efficiency & Losses



Efficiency PMP31242 Rev A (40V-FET)

input voltage range 8.5V to 17V

output voltage selectable 17V / 19V

allows peak currents up to 2.5A

losses <1W at max. current 1.5A

flat efficiency 95%+ 500mA to 2.5A load current



PMP31242 Design Review – Ripple Voltages

Ripple and Noise PMP31242 Rev A



Input Voltage Ripple

Output Voltage Ripple

Reflected ripple and output voltage ripple at 20mV / division, **20MHz bandwidth**; ripple <5mVpp and noise <30mVpk - in time domain looks promising,

but what about frequency domain ?





PMP31242 Design Review – CISPR 25 class 5



but peak at 14 MHz, 2000 bandstRuments

PMP31242 Design Review – CISPR 25 class 5



Noise Floor 150kHz to 30MHz,

- peak at 14 MHz still there...
- LW band, 150kHz to 300kHz
- MW band, 530kHz to 1.8MHz
- 49m band, 5.9MHz to 6.2MHz
- CB band, 26MHz to 28MHz

no limits for HAM bands 160m to 10m



Agenda

- Funkstation
- Versorgungskonzept PMP31210 (+ PMP31242)
- End Fed Antenne
- Felderprobung

Nachteile, IC-706 (20 Jahre alt !)

- hohe Stromaufnahme RX, >1A
- keine Wasserfallanzeige, kein Display-Ausgang
- kein integrierter Tuner
- kein isoliertes i/f
- mangelhafte Grossignalfestigkeit an langen Antennen (jedoch klein, und deckt HF/50m/2m/70cm ab)
- > IC-7300 (int. Tuner / int. I/F, 4.2kg) + Alinco DM-330 (2.5kg)



